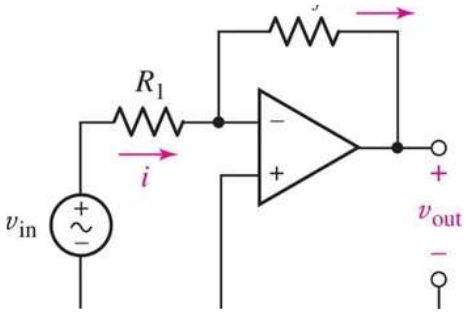


Kahoot

The Operational Amplifier

Questions (10)

1 - Quiz

Which of the following op amps is not a modern op amp?


▲ 


◆ 


● 


2 - Quiz

Which of the following circuits is not a negative feedback configuration?

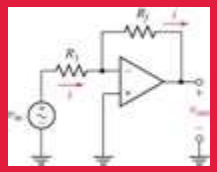▲ 

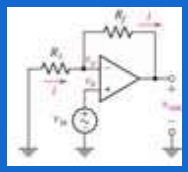
◆ 

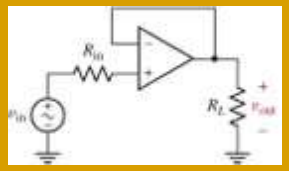● 

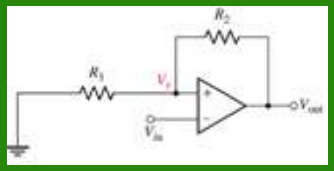■ 

3 - Quiz

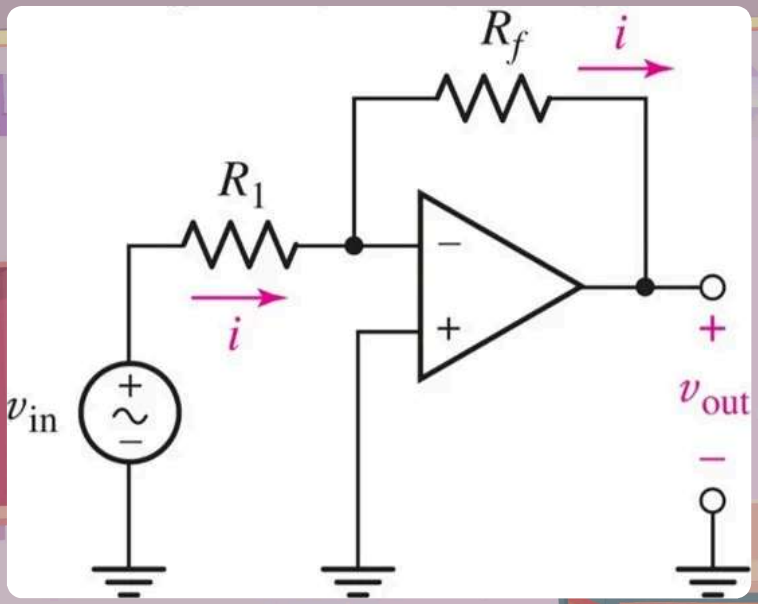If V_{in}=1V, R_f=2Ω, R_1=1Ω, what is the output voltage?



▲ 1V


◆ 2V

● -1V

■ -2V ✓

4 - True or false

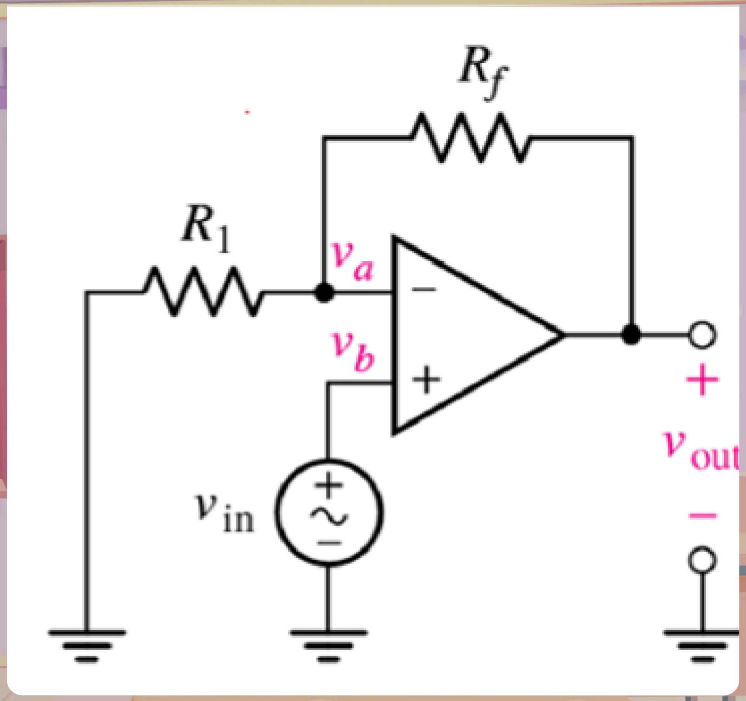
The non-inverting amplifier can work as an attenuator.



◆ True


▲ False ✓

5 - True or false

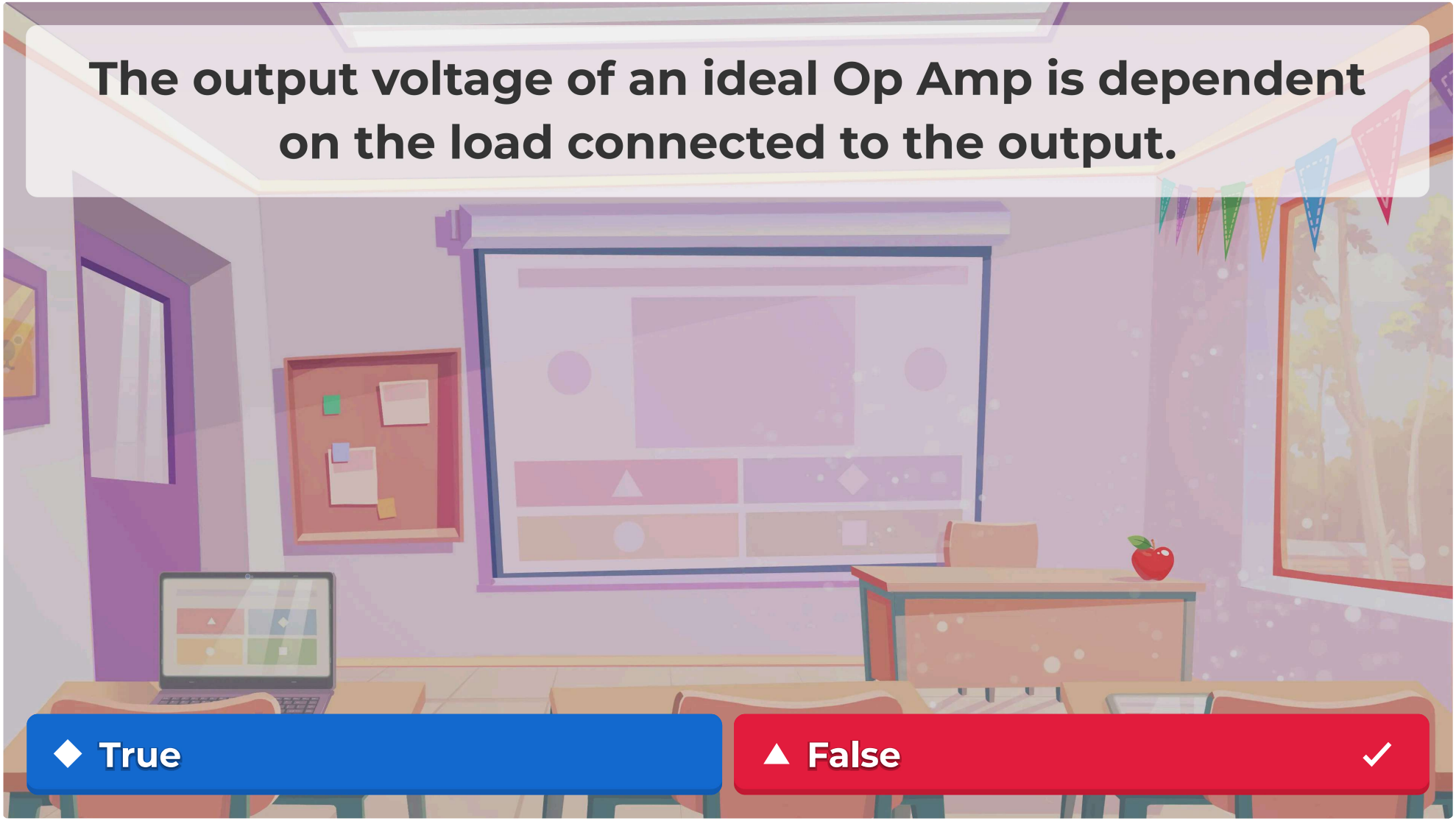

6 - Quiz

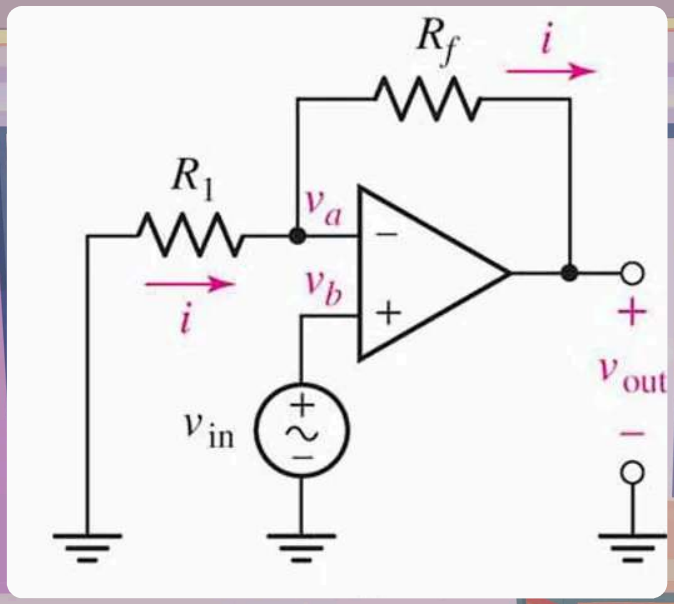What is the input impedance of the following circuit?



▲ ∞ ✓


◆ R_1

● R_f

■ $1+R_f/R_1$

7 - Quiz

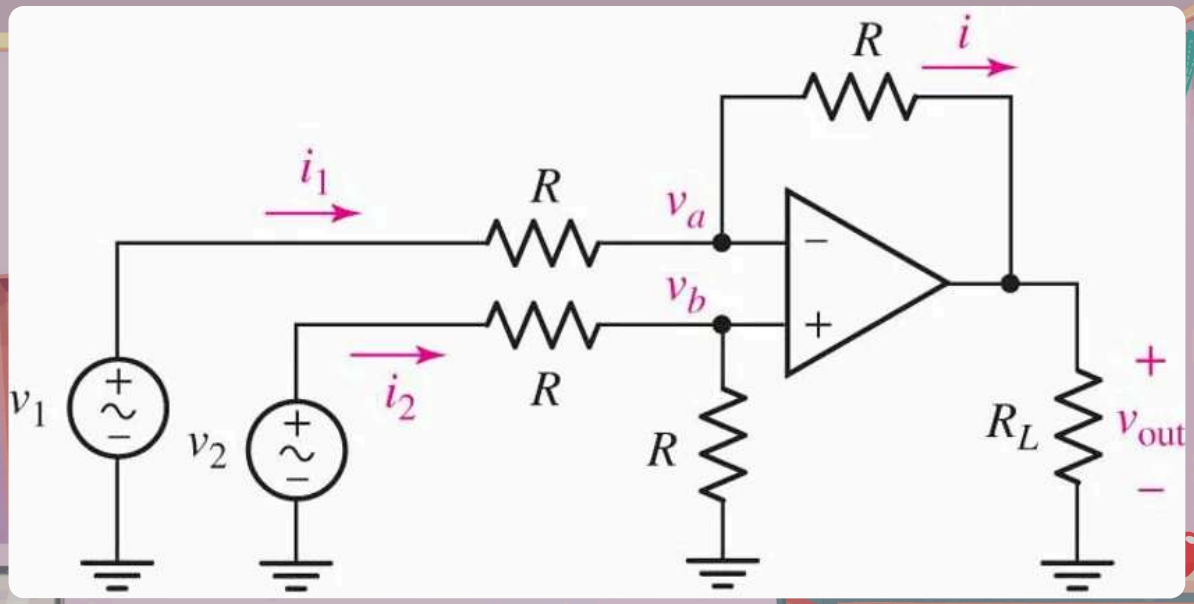If v_1=1V, v_2=3V, what is the output voltage?



▲ 1V


◆ 2V ✓

● 3V

■ 4V

8 - True or false

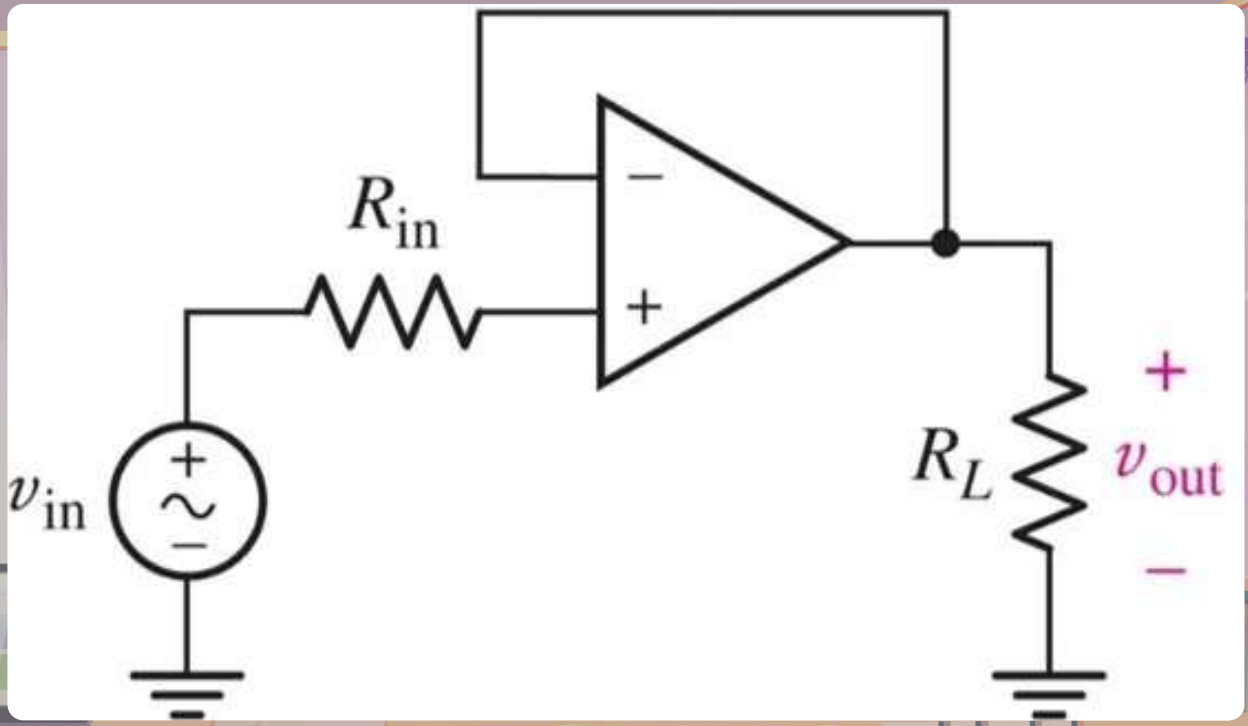The Op Amp circuit is a non-inverting amplifier.




◆ True ✓

▲ False

9 - Quiz

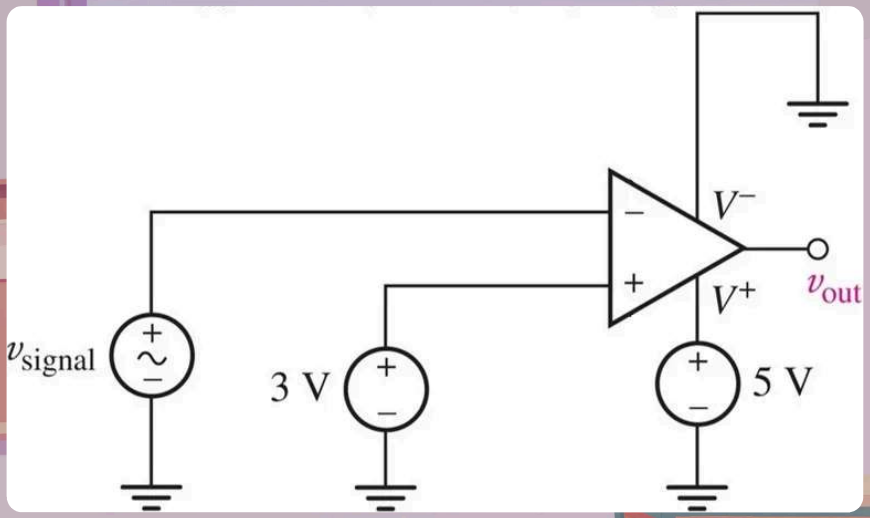If the input voltage is 2V of the following cirucit, what is the output voltage?



▲ 1V


◆ 0V

● 5V ✓

■ -1V

10 - Quiz

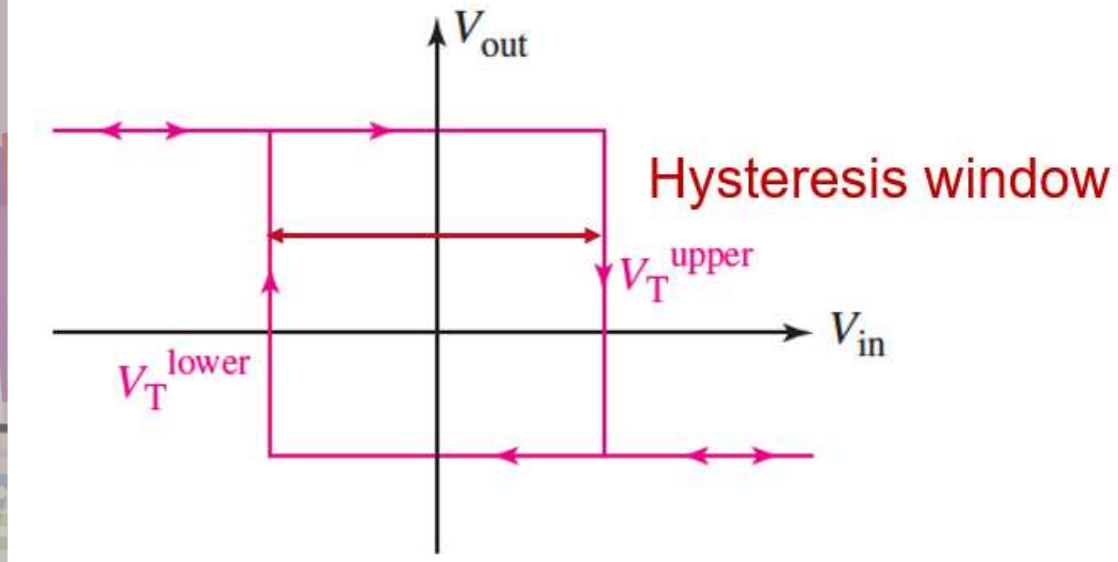if the input voltage changes within the hystersis window, will the output voltage change?



▲ Yes

◆ No ✓