
Tutorial question 1

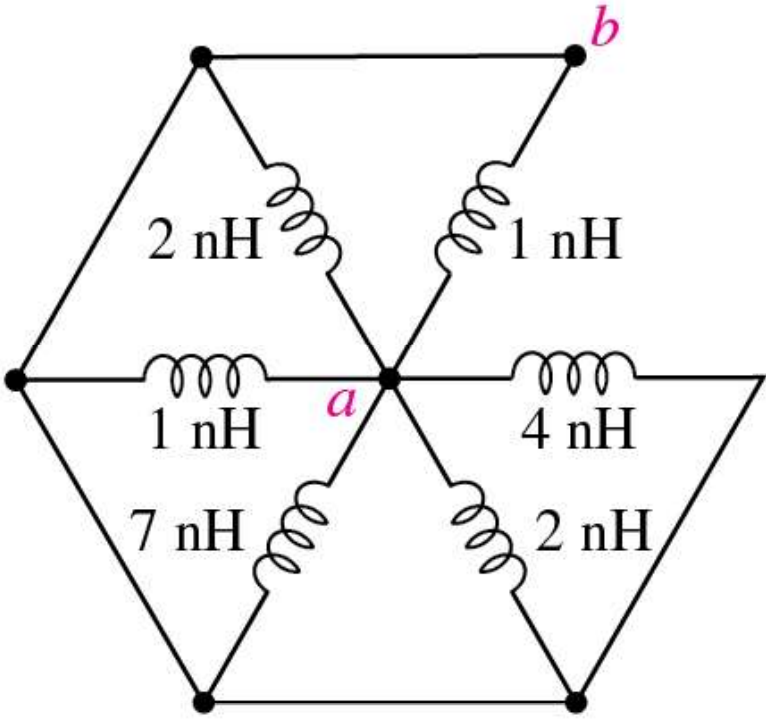A 100 mH inductor has voltage v_L=$2e^{-3t}$V across its terminals. Determine the resulting inductor current if $i_L(-0.5) = 1\text{A}$.




Tutorial question 2

Determine the equivalent inductance seen looking into the terminals marked a and b of the network represented below.




Tutorial question 3

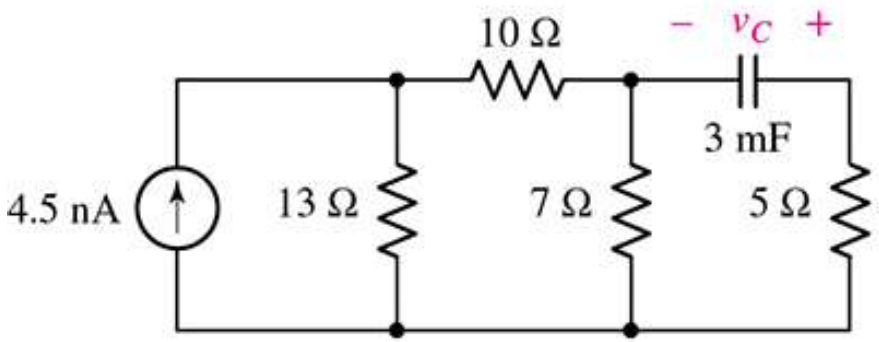For each circuit shown in Figure below, calculate the voltage labeled v_c.



(a)

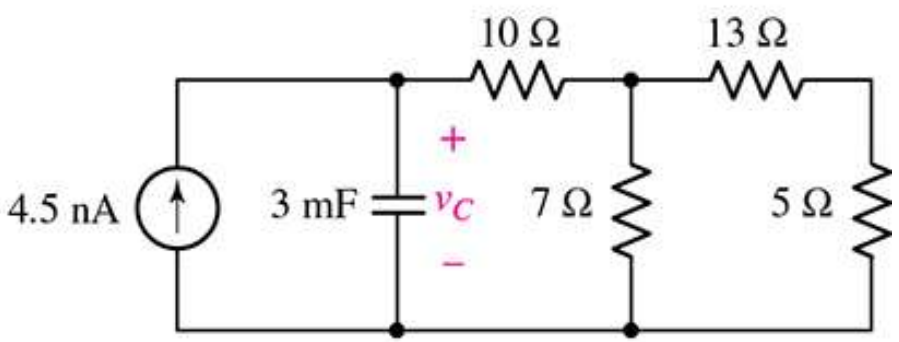

(b)