
Tutorial Question 1 (Example 4 continued)

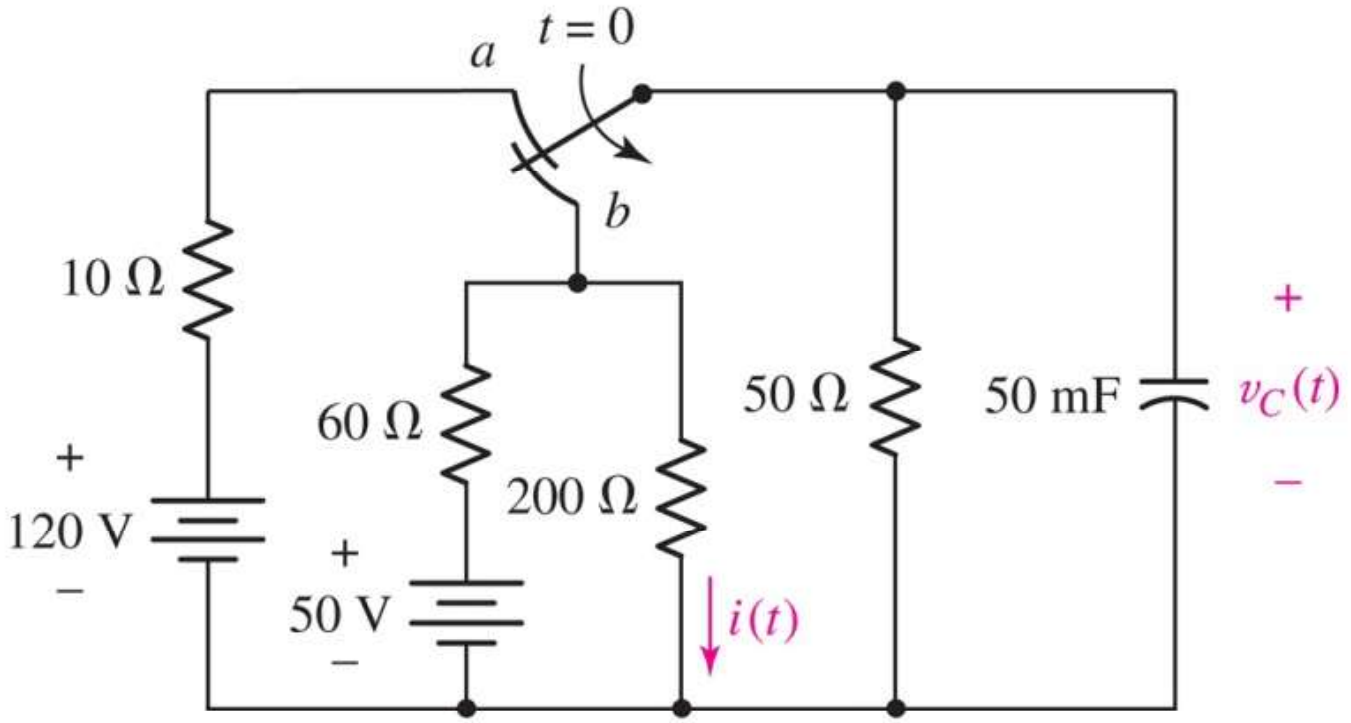Find the current $i(t)$ through the 200Ω resistor all the time.



Tutorial question 2

A voltage source, $v_s = 20u(t)$ V, is in series with a 200 Ω resistor and a 4 H inductor. Find the magnitude of the inductor current at t equal to (a) 0^-; (b) 0^+; (c) 8 ms; (d)15 ms.

