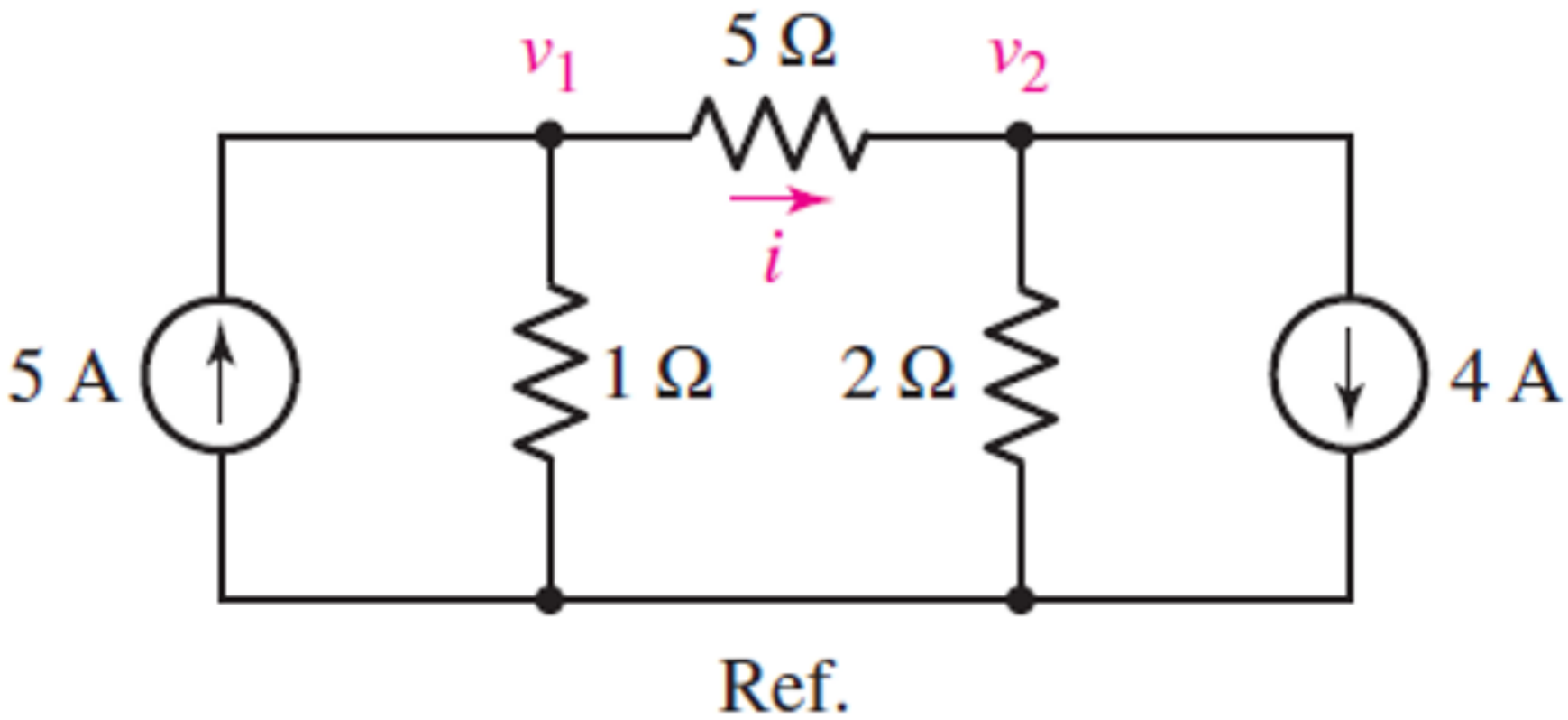
Q1: In the circuit below, determine the current labeled i with the assistance of nodal analysis techniques.



Q2: Given the circuit below:

(a) Employing mesh analysis procedures, obtain a value for the current labeled i in the circuit below

(b) Calculate v1 and v2

(c) In nodal analysis, we treat the entire wire as a singular node, However, does it make any sense that there could be a flow of current from 1 to 2 in this scenario? And why?

